

Division 6 - Lincoln Laboratory  
 Massachusetts Institute of Technology  
 Lexington 73, Massachusetts

SUBJECT: TRANSISTOR CIRCUITS COURSE  
 Number 4. Transistor Amplifiers

To: Distribution List

From: Donald J. Eckl

Date: August 19, 1955

Approved: William N. Papian

Abstract: Three usable amplifier configurations exist for the junction transistor. The grounded-base amplifier has the highest frequency response. The grounded-emitter has the largest power gain. The grounded-collector or emitter follower serves as an impedance transformer much in the way of a vacuum tube cathode follower. These circuits have many important differences from their vacuum tube counterparts. An important one is the more marked effect of source and load impedances on their performance. Input and output circuits are not isolated by the transistor.

1.0 Grounded-base amplifier

Suppose we consider the grounded-base circuit shown in Fig. 1.

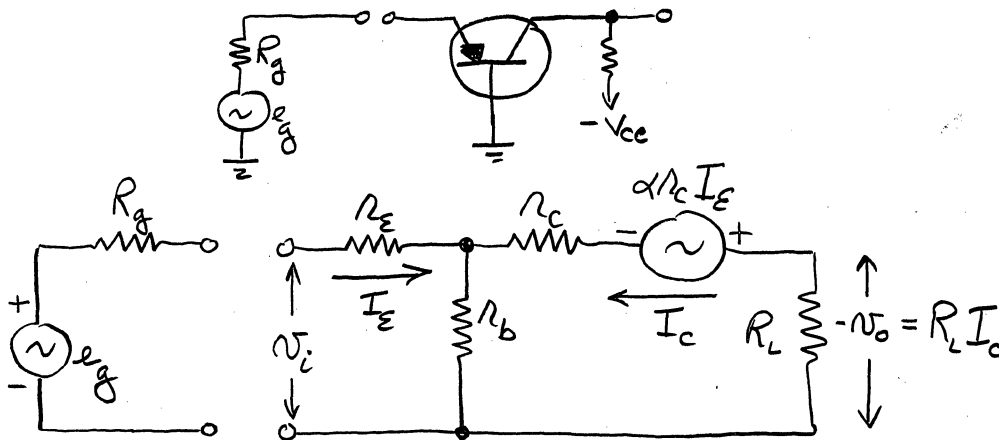


FIG. 1 - GROUNDED BASE TRANSISTOR AMPLIFIER

The circuit equations are:

$$v_i = I_e(r_e + r_b) + I_c r_b.$$

$$0 = I_e(\alpha r_c + r_b) + I_c(r_c + r_b + R_L).$$

The determinant is

$$\Delta = \begin{vmatrix} (r_e + r_b) & r_b \\ (\alpha r_c + r_b) & (r_c + r_b + R_L) \end{vmatrix}$$

or 
$$\Delta = r_b [r_e + r_c(1-\alpha) + R_L] + r_e(r_c + R_L). \quad (1)$$

$$\Delta \cdot I_e = \begin{vmatrix} v_i & r_b \\ 0 & r_c + r_b + R_L \end{vmatrix}$$

$$I_e = \frac{v_i}{\Delta} (r_c + r_b + R_L) \quad (2)$$

$$\Delta \cdot I_c = \begin{vmatrix} r_e + r_b & v_i \\ \alpha r_c + r_b & 0 \end{vmatrix}$$

$$I_c = -\frac{v_i}{\Delta} (\alpha r_c + r_b) \quad (3)$$

The voltage gain is given by:

$$G_v = \frac{-I_c R_L}{v_i} = \frac{(\alpha r_c + r_b) R_L}{\Delta}.$$

There is no phase inversion in the grounded-base circuit. The current gain is given by:

$$A = \frac{I_c}{I_e} = \frac{\alpha r_c + r_b}{r_c + r_b + R_L}.$$

Note that for a short-circuited output ( $R_L = 0$ ) this is simply  $\alpha$ .

The input resistance is  $R_i = v_i / I_e$ .

$$\therefore R_i = \frac{\Delta}{r_b + r_c + R_L}.$$

$$\text{or } R_i = r_e + r_b \left[ \frac{r_c(1-\alpha) + R_L}{r_c + r_b + R_L} \right].$$


Note that the input resistance depends on the collector load  $R_L$ .

The power gain of the circuit is  $I_c^2 R_L / I_e^2 R_i$ .

$$P.G. = A^2 \left( \frac{R_L}{R_i} \right).$$

This expression shows quite clearly how it is possible to have a power gain in the grounded-base circuit even though the current gain is less than unity. The input impedance is of the order of  $r_e + r_b \approx 300 \Omega$  while the output load  $R_L$  may be several thousand ohms. It is the higher impedance level of the output circuit which provides the power gain.

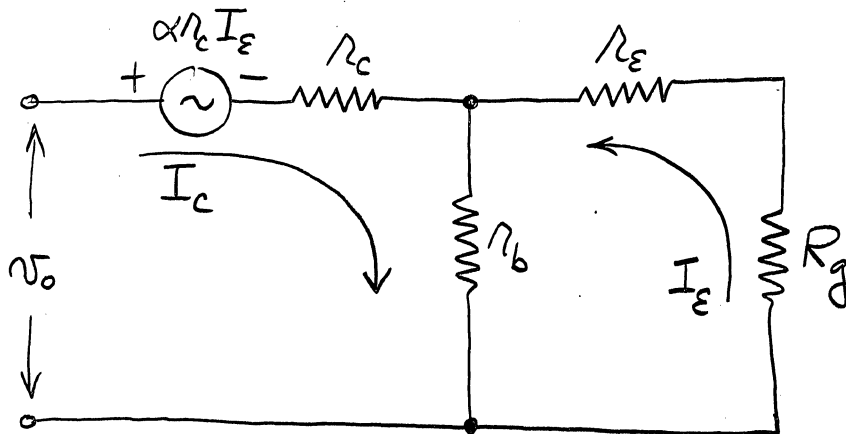To get the output resistance of the grounded-base stage we must apply a voltage to the output terminals and calculate  $I_c$ .



$$\begin{cases} 0 = (R_g + r_e + r_b)I_e + r_b I_c. \\ v_o = (\alpha r_c + r_b)I_e + (r_b + r_c)I_c. \end{cases}$$

$$\Delta = r_c(r_e + r_c + R_g) + r_b(R_g + r_e - \alpha r_c).$$

$$\Delta \cdot I_c = \begin{vmatrix} (R_g + r_e + r_b) & 0 \\ (\alpha r_c + r_b) & v_o \end{vmatrix}.$$

The output resistance is  $v_o/I_c$ .

$$\therefore R_o = r_c - r_b \left( \frac{\alpha r_c - r_e - R_g}{r_e + r_b + R_g} \right) .$$

The output resistance depends on the generator resistance  $R_g$ .

If we now make some assumptions about the relative sizes of the quantities in the above expressions, we can obtain simplified versions. Assume:

$$r_c(1-\alpha) \gg R_L \gg r_e, r_b .$$

Then, 
$$\Delta = r_c [r_e + r_b(1-\alpha)] .$$

$$G_v = \frac{\alpha R_L}{r_e + r_b(1-\alpha)} .$$

$$A = \alpha$$

$$R_i = r_e + r_b(1-\alpha) .$$


$$R_o = r_c \left\{ \frac{r_e + r_b(1-\alpha) + R_g}{r_e + r_b + R_g} \right\} \approx r_c .$$

$$P.G. = \frac{\alpha^2 R_L}{r_e + r_b(1-\alpha)}$$

## 2.0 Grounded-emitter Amplifier

The grounded-emitter circuit is shown in Fig. 2.

FIG. 2a

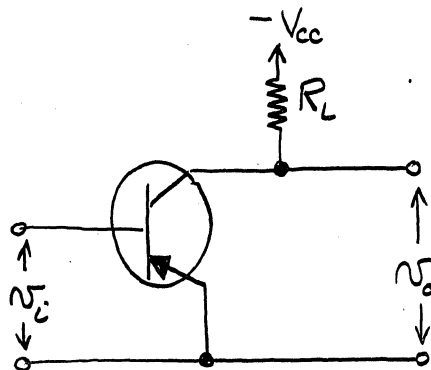

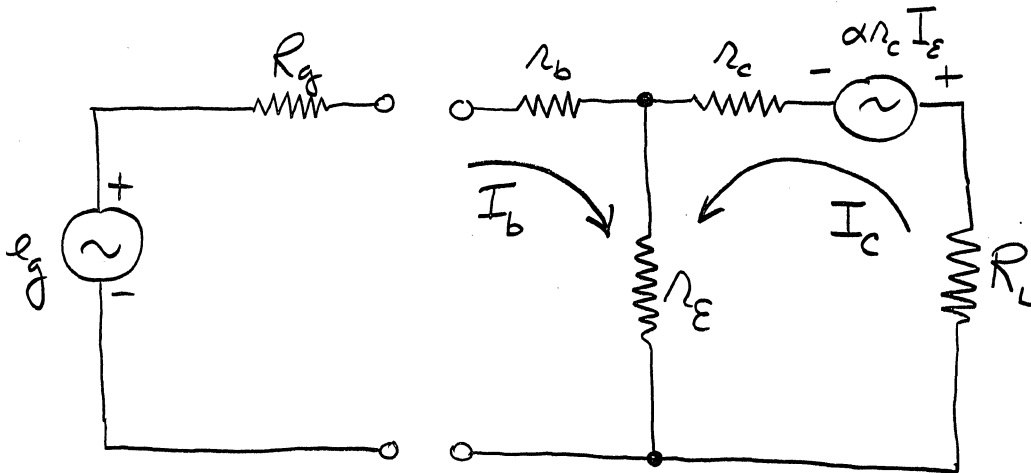


FIG. 2b - GROUND-EMITTER AMPLIFIER

$$e_g = (R_g + r_b + r_e) I_b + r_e I_c.$$

$$0 = \alpha r_c (-I_b - I_c) + r_e I_b + (R_L + r_c + r_e) I_c.$$

$$0 = (r_e - \alpha r_c) I_b + \{R_L + r_e + r_c(1-\alpha)\} I_c.$$

$$\Delta = r_b \{r_e + R_L + r_c(1-\alpha)\} + r_e (r_c + R_L).$$

This is, of course, the same as for the grounded-base circuit.

$$I_b = \frac{v_i}{\Delta} \{r_e + R_L + r_c(1-\alpha)\}.$$

$$I_c = \frac{v_i}{\Delta} (\alpha r_c - r_e).$$

The voltage gain for the grounded-emitter circuit is

$$G_v = \frac{-I_c R_L}{v_i} = \frac{-(\alpha r_c - r_e) R_L}{\Delta}.$$

There is a phase inversion in the output signal. The current gain is given by:

$$A = \frac{I_c}{I_b} = \frac{\alpha r_c - r_e}{r_c(1-\alpha) + r_e + R_L}.$$

The input resistance of the grounded emitter circuit is

$$R_i = r_b + r_e \left\{ \frac{r_c + R_L}{r_c(1-\alpha) + r_e + R_L} \right\}.$$

The power gain is

$$P.G. = A^2 \left( \frac{R_L}{R_i} \right).$$

In this case  $A > 1$  so the power gain is larger than for the grounded base circuit.

If the output resistance is calculated as before the result is

$$R_o = r_c(1-\alpha) + r_e \left\{ \frac{R_g + r_b + \alpha r_c}{R_g + r_b + r_e} \right\}.$$

If we assume that

$$r_c(1-\alpha) \gg R_L \gg r_e, r_b$$

we obtain the following approximations:

$$G_v = \frac{-\alpha R_L}{r_e + r_b(1-\alpha)}$$

$$A = \frac{\alpha}{1-\alpha}$$

$$R_i = r_b + \frac{r_e}{1-\alpha}.$$

$$R_o = r_c(1-\alpha) + r_e \left\{ \frac{\alpha r_c + R_g}{r_e + r_b + R_g} \right\}$$

$$P.G. = \frac{1}{(1-\alpha)} \cdot \frac{\alpha^2 R_L}{\{r_e + r_b(1-\alpha)\}}$$

### 3.0 Grounded-Collector Amplifier

The grounded-collector amplifier is shown in Figure 3. This is the transistor equivalent of the cathode-follower and is frequently referred to as an emitter-follower.

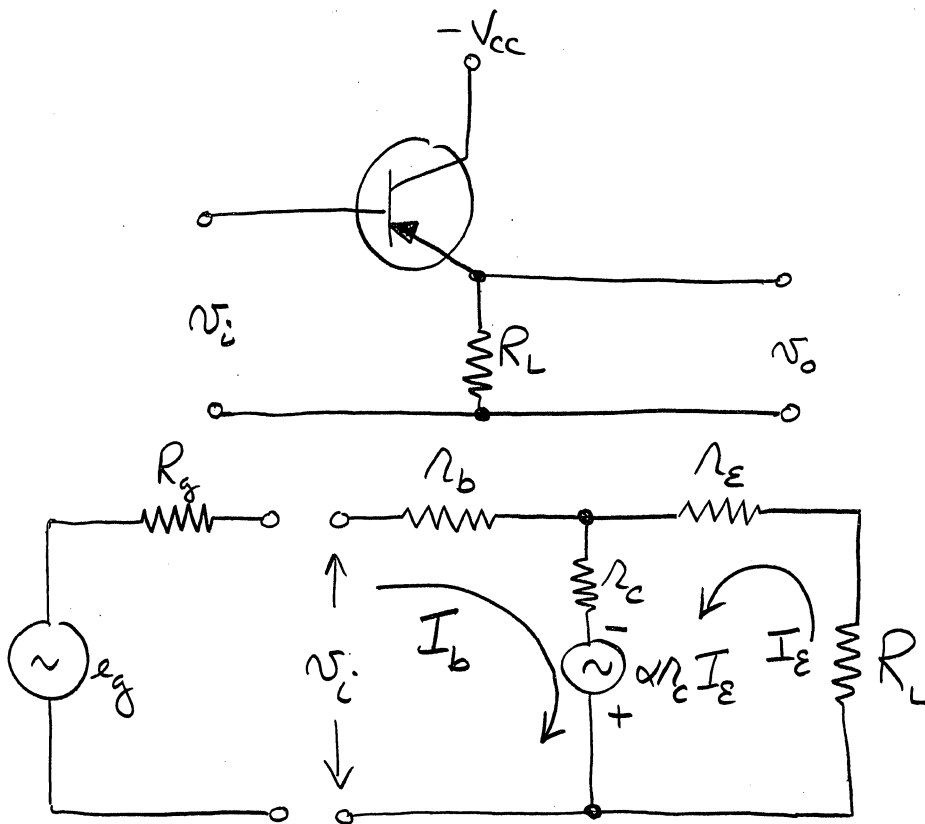


FIG. 3 - GROUNDED - COLLECTOR AMPLIFIER

The loop equations are:

$$v_i = (r_b + r_c) I_b + r_c(1-\alpha)I_e$$

$$0 = r_c I_b + \{R_L + r_e + r_c(1-\alpha)\} I_e.$$

The input or base current is:

$$I_b = \frac{v_i}{\Delta} \left\{ r_c(1-\alpha) + r_e + R_L \right\}$$

The output current is:

$$I_e = \frac{v_i}{\Delta} r_c.$$

The voltage gain for the emitter-follower is

$$G_v = \frac{I_e R_L}{v_i} = \frac{r_c R_L}{\Delta}$$

The current gain is normally greater than unity.

$$A = \frac{I_c}{I_e} = \frac{r_c}{r_c(1-\alpha) + r_e + R_L} \circ$$

The input resistance is

$$R_i = r_b + r_c \left\{ \frac{r_e + R_L}{r_c(1-\alpha) + r_e + R_L} \right\}$$

Note that this is approximately  $R_L/1-\alpha$  which is an order of magnitude larger than the emitter resistance  $R_L$ .

The power gain is  $A^2 \left( \frac{R_L}{R_i} \right)$  which is greater than unity because of the  $A^2$  term.

The output resistance is given by

$$R_o = r_e + r_c(1-\alpha) \left\{ \frac{R_g + r_b}{R_g + r_b + r_c} \right\}$$

If we make the same assumptions as before, we obtain the following approximations:

$$G_v = 1$$

$$A = \frac{1}{1-\alpha} = \beta + 1$$

$$R_i = R_L / (1-\alpha) = R_L (\beta + 1)$$




$$P.G. = \frac{1}{1-\alpha} = \beta + 1$$

$$R_o = r_e + (r_b + R_g)(1-\alpha).$$

Note that the circuit has a relatively high input resistance and low output resistance.

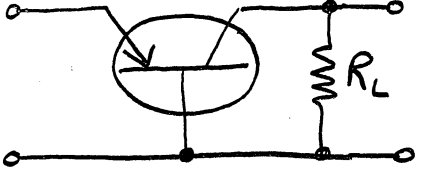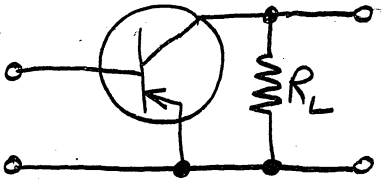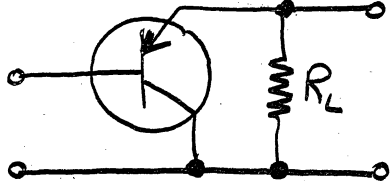A comparison of approximate formulae for the three configurations is given in Fig. 4.



<p>FIGURE 4</p> <p>APPROX. FORMULAE ASSUMING</p> <p><math>r_c(1-\alpha) \gg R_L \gg r_e, r_b</math></p>	<p>Grounded-base</p> 	<p>Grounded-emitter</p> 	<p>Grounded-collector</p> 
<p>CURRENT GAIN</p>	<p><math>\alpha</math></p>	<p><math>\frac{\alpha}{1-\alpha} = \beta</math></p>	<p><math>\frac{1}{1-\alpha} = \beta + 1</math></p>
<p>POWER GAIN</p>	<p><math>\frac{\alpha^2 R_L}{r_e + r_b (1-\alpha)}</math></p>	<p><math>\left( \frac{1}{1-\alpha} \right) \left\{ \frac{\alpha^2 R_L}{r_e + r_b (1-\alpha)} \right\}</math></p>	<p><math>\frac{1}{1-\alpha} = \beta + 1</math></p>
<p>INPUT RESISTANCE</p>	<p><math>r_e + r_b (1-\alpha)</math></p>	<p><math>r_b + \frac{r_e}{1-\alpha}</math></p>	<p><math>\frac{R_L}{1-\alpha} = (\beta + 1) R_L</math></p>
<p>OUTPUT RESISTANCE</p>	<p><math>r_c \left\{ \frac{r_e + R_g + r_b (1-\alpha)}{r_e + R_g + r_b} \right\}</math></p>	<p><math>r_c (1-\alpha) + r_e \left\{ \frac{\alpha r_c + R_g}{r_e + r_b + R_g} \right\}</math></p>	<p><math>r_e + (r_b + R_g) (1 - \alpha)</math></p>
<p>VOLTAGE GAIN</p>	<p><math>\frac{\alpha R_L}{r_e + r_b (1-\alpha)}</math></p>	<p><math>-\frac{\alpha R_L}{r_e + r_b (1-\alpha)}</math></p>	<p>1</p>

4.0 Effect of Load Resistance on Amplifier Performance

In general we are not at liberty to change the internal transistor parameters given in the previous expressions. We can, however, vary the load  $R_L$ .

Fig. 5 shows the effect of load resistance on current gain for the 3 amplifiers.

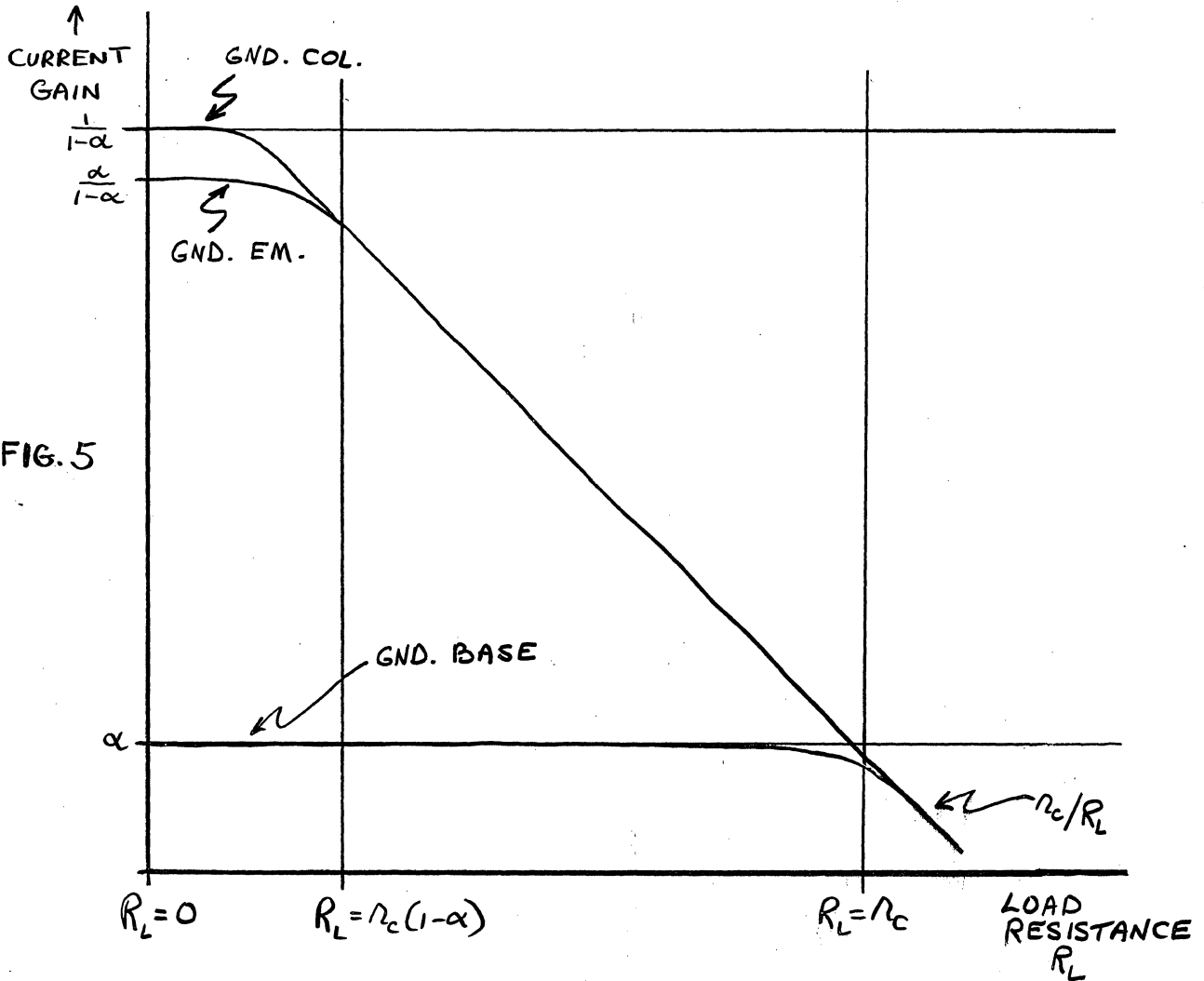


FIG. 5

As  $R_L$  becomes greater than  $r_c$  all three have a current gain of about  $r_c/R_L$ .

The effect of load resistance on input resistance is shown in Figure. 6.


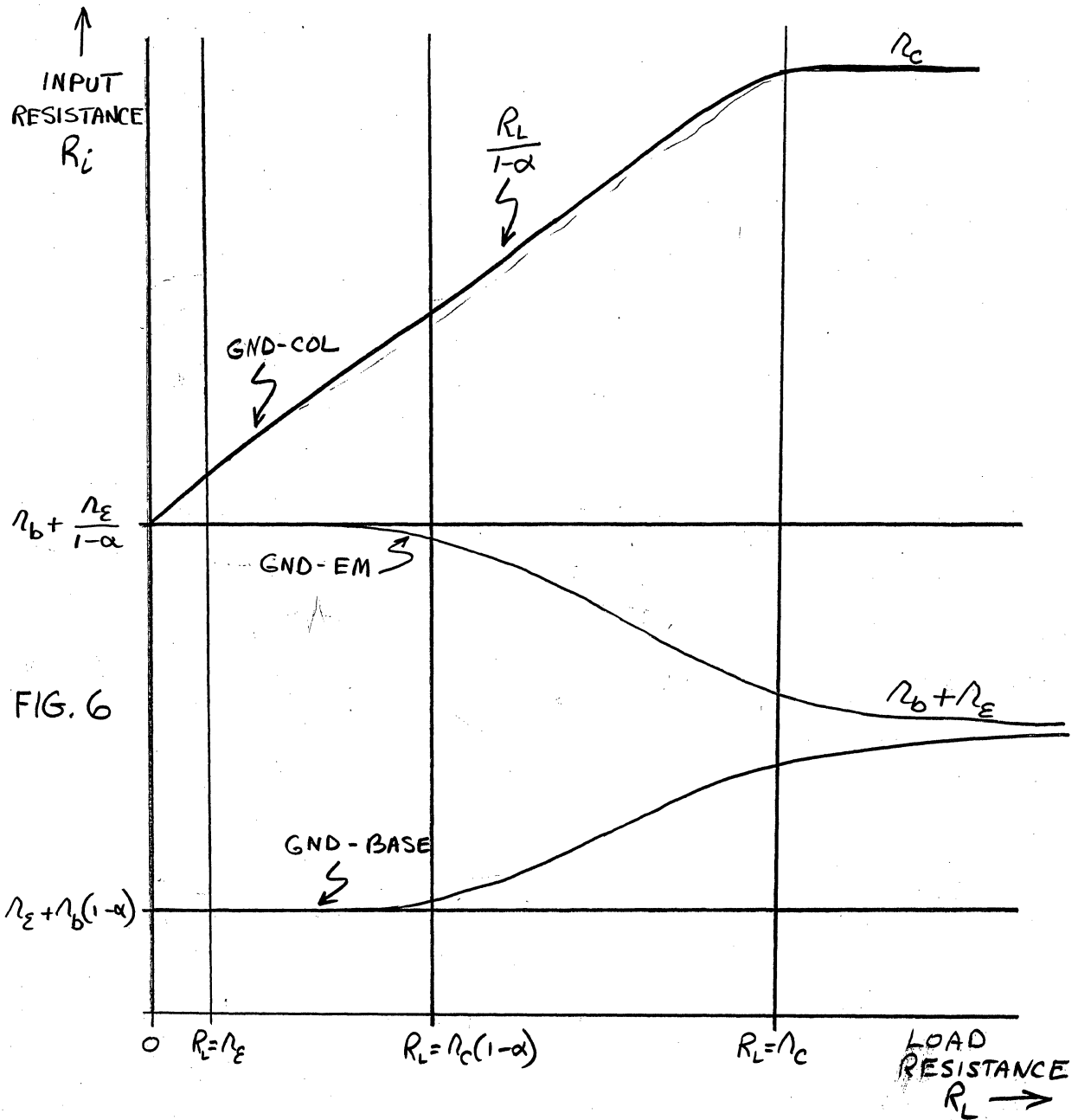


FIG. 6

The effect of the driving generator impedance on the output impedance of a transistor stage is shown in Figure 7. It is important to note the difference in current and voltage drive on the output impedance.

FIG. 7

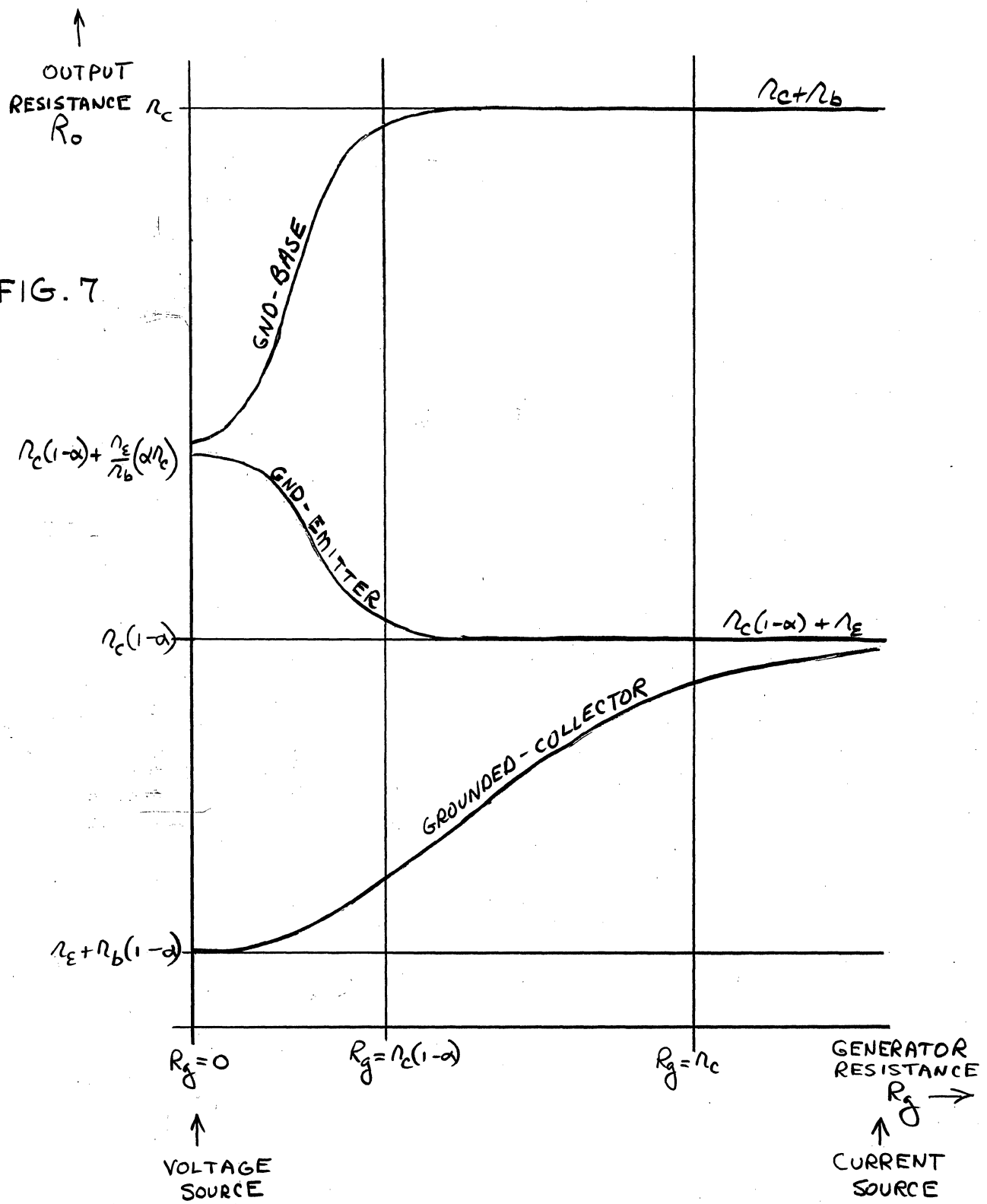

### 5.0 Frequency Response of Transistor Amplifiers

This is a subject which will be treated in more detail later on. The frequency response of the grounded-base amplifier is due to the variation in current-gain  $\alpha$  with frequency. This can be expressed approximately as:

$$\alpha = \frac{\alpha_0}{1 + j \left( \frac{f}{f_{c\alpha}} \right)}$$

where  $\alpha_0$  is the low frequency  $\alpha$  and  $f_{c\alpha}$  is the frequency at which  $\alpha$  is  $.707\alpha_0$ . This expression is only an approximation and, in fact, one which is accurate only for  $f/f_{c\alpha} \leq 1$ .

The current gain of a grounded-emitter stage is

$$\beta = \frac{\alpha}{1-\alpha} = \frac{\frac{\alpha_0}{1 + j \left( \frac{f}{f_{c\alpha}} \right)}}{1 - \frac{\alpha_0}{1 + j \left( \frac{f}{f_{c\alpha}} \right)}} = \frac{\alpha_0}{1 - \alpha_0 + j \left( \frac{f}{f_{c\alpha}} \right)}$$

If we now divide top and bottom by  $1 - \alpha_0$  we get


$$\frac{(\alpha_0/1 - \alpha_0)}{1 + j \frac{f}{f_{c\alpha} (1 - \alpha_0)}}$$

or

$$\beta = \frac{\beta_0}{1 + j \frac{f}{f_{c\alpha} (1 - \alpha_0)}}$$

Therefore the grounded-emitter stage has a frequency response  $(1 - \alpha_0)$  times that of the grounded-base circuit. This may be 1/10 or less.

The next chapter will discuss temperature stability of transistors.

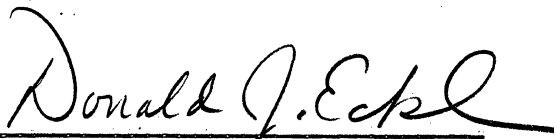  
Donald J. Eckl

Distribution List

1. Ayer, W, B-122
2. Barrett, B, B-135
3. Best, R, B-129
4. Bradspies, S., B-170
5. Brown, D. R., C-139
6. Burke, R., B-171
7. Buzzard, R., B-121
8. Cerier, M. - C-141
9. Cohler, E.U., B-147
10. Daggett, N., C-141
11. Davidson, G., B-170
12. Eckl, D.J., B-147
13. Epstein, IO-397
14. Fadiman, J., B-191A
15. Fergus, P., B-171A
16. Forgie, J. C-141
17. Freeman, J.R., B-147
18. Gloor, R. D., B-171
19. Glover, E., B-141
20. Grennell, A., B-183
21. Griffith, IO-397
22. Highleyman, W., B-171
23. Hudson, B., D-243
24. Hudson, M., C-309
25. Hughes, R., B-191
26. Jedynak, L., IO-397
27. Jones, N.T., B-121
28. Kirk, C.T., B-147
29. Konkle, K., B-147
30. MacDonald, A., B-191
31. Meisling, T., B-181
32. Ockene, N., B-141
33. Olsen, K., B-191A
34. Parfenuk, D., B-191
35. Petersen, M., B-191
36. Pugh, A. L., B-181
37. Richardi, B-191
38. Santelman, B-135
39. Sarles, F., B-170
40. Sawyer, R., B-191
41. Shansky, D., B-135
42. Sokal, Et., B-309H
43. Tessari, D-243
44. Theriault, C-309
45. White, P., B-171
46. Woolf, B-132
47. Ziemann, H., B-132
48. Zopatti, R., B-186